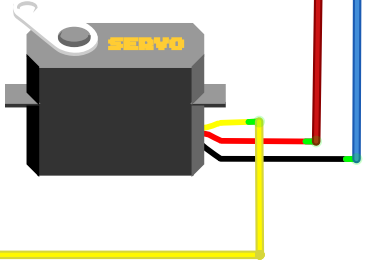


These 4 pins will connect to I2C LCD display (SCL to SCL, SDA to SDA, GND and VCC to common GND and VCC on breadboard)

These 6 pins will connect to 4-channel relay (GND to common GND, VCC to common VCC on breadboard, 10,11,12,13 to IN1, IN2, IN3, IN4)



These 5 pins will connect to Max6675 Temperature Sensor (GND to common GND on breadboard, VCC to 3.3V on Arduino, DO, CS, CLK to pin 4,5,6 on Arduino)