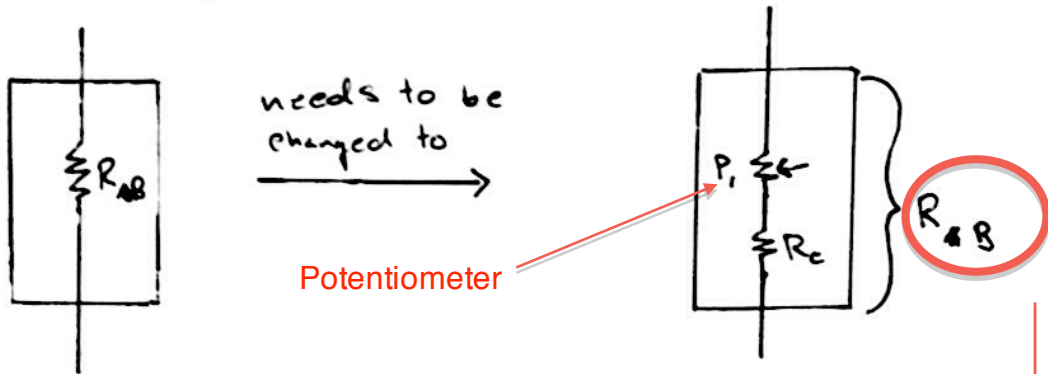


So that means if $R_B C \approx 1.44s$, C needs to be around $C \approx \frac{1.44s}{44.3E3\Omega} \approx 33\mu F$ (a standard value!)
 Which I didn't have but that's okay

Because the potentiometer actually goes to zero resistance the duty cycle will be effected if there is no resistor in place of R_B . I now refer to box 1.



Where the order of P_1 and R_c don't actually matter.

Calculations with final resistor and Pot. values

Values: $P_1 = 44.3K$, $R_c = 9.88K$, $R_A = 153.5$, $C = 47\mu F$

Values were measured using a multimeter

When P_1 is at full crank ($P_1 = 44.3K$) $R_B = P_1 + R_c$ (Box 1)

$R_B = 54.18K$

Pot. @ Full Crank

$$D_{Pon} = \frac{R_B}{R_A + (2R_B)} = \frac{54.18K}{153.5 + (2 \cdot 54.18K)} = 0.499 \approx 50\%$$

$$t_{on}^{(calc)} = 0.693 (153.5 + 54.18E3) 33E-6 = 1.2s [w/47\mu F; 1.8s]$$

$$t_{off}^{(calc)} = 0.693 (54.18E3) 33E-6 = 1.2s [w/47\mu F; 1.8s]$$

When $P_1 = 0$, $R_B = R_c = 9.88K$

Pot @ ~0Ω

$$t_{on}^{(calc)} = 0.693 (153.5 + 9.88K) 33E-6 = 0.229s [w/47\mu F; 0.3s]$$

$$t_{off}^{(calc)} = 0.693 (9.88K) 33E-6 = 0.226 [w/47\mu F; 0.3s]$$

$$D_{Poff} \approx 50\%$$

Actual capacitance values were variable