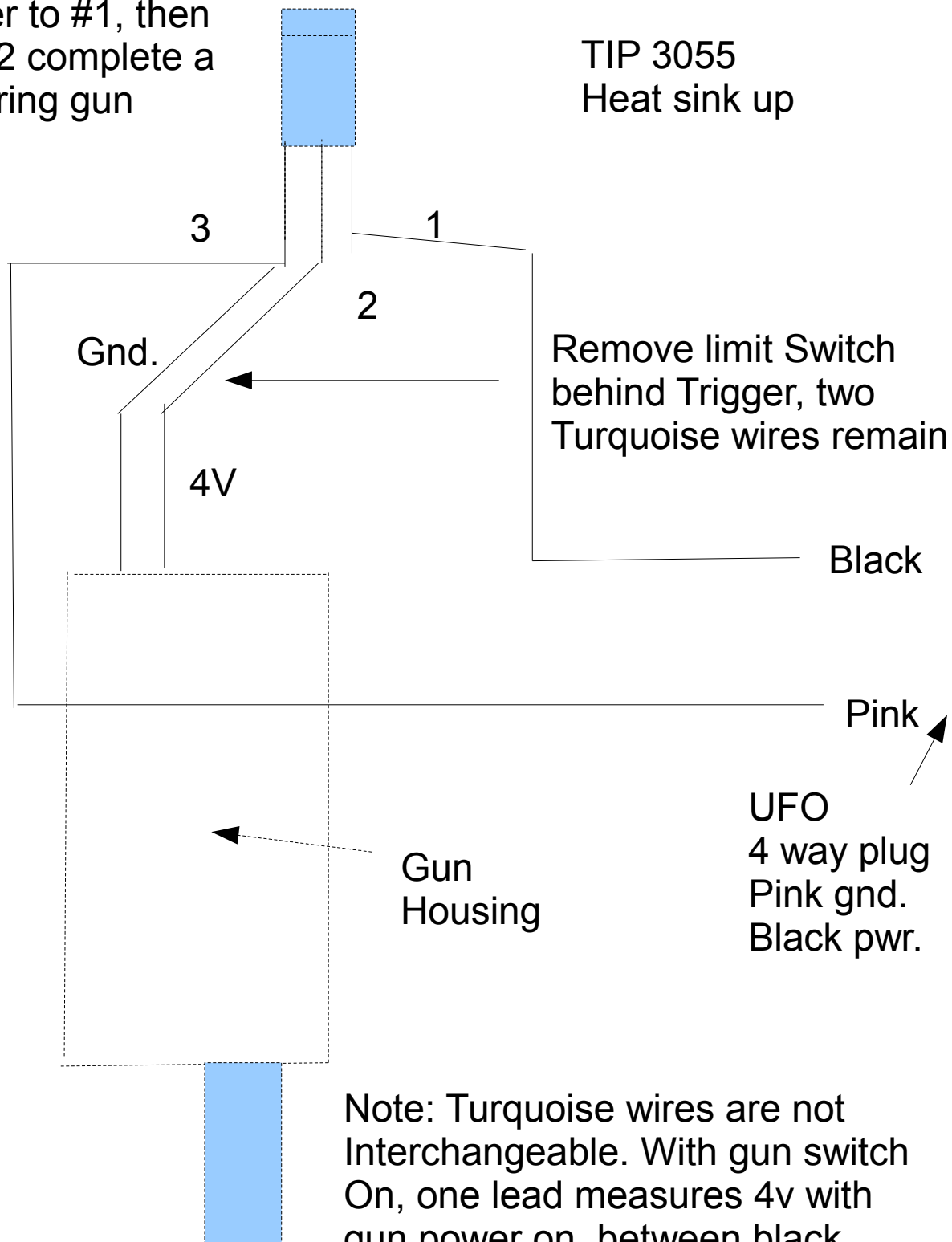


1 Base
 2 Collector
 3 Emitter, when we
 Put power to #1, then
 #2 and #2 complete a
 Circuit, firing gun



Note: Turquoise wires are not
 Interchangeable. With gun switch
 On, one lead measures 4v with
 gun power on, between black
 UFO lead and turquoise lead. It
 goes to Collector, #2 on transistor